
Lecture24


Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

How to describe a circuit

- Of course, we can draw a circuit schematic. What else?
- A netlist for this circuit looks like:

```
va out 0 1.0  
r1 out 0 1000
```

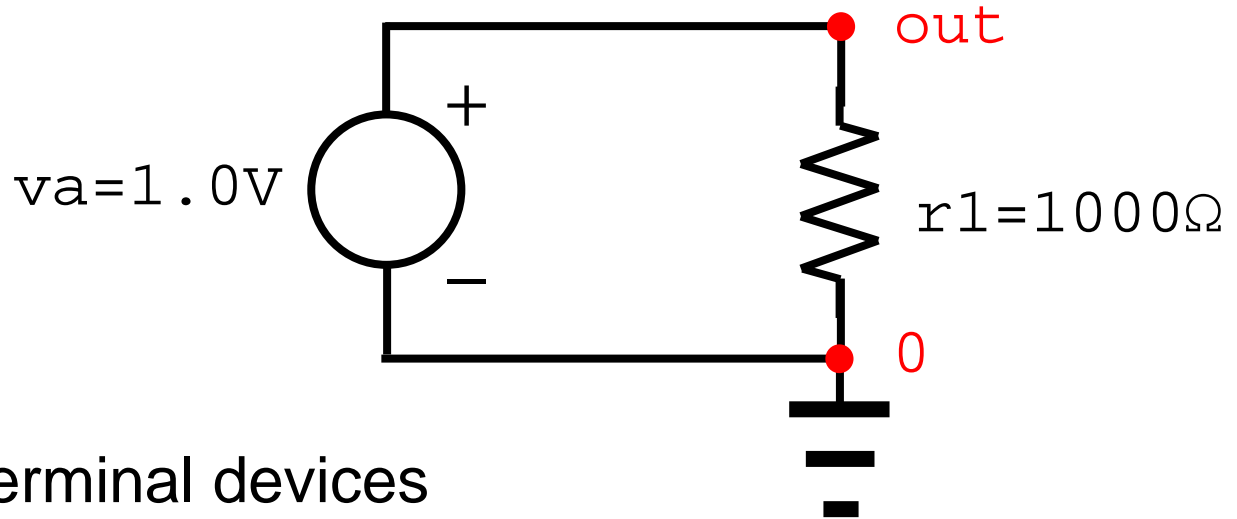

- Format for two-terminal devices
elementlabel node1 node2 value


RC filter

- A netlist for this circuit looks like:

```
c1 in out 5e-12
```


```
r1 out 0 2e6
```

```
vin in 0 1.5
```

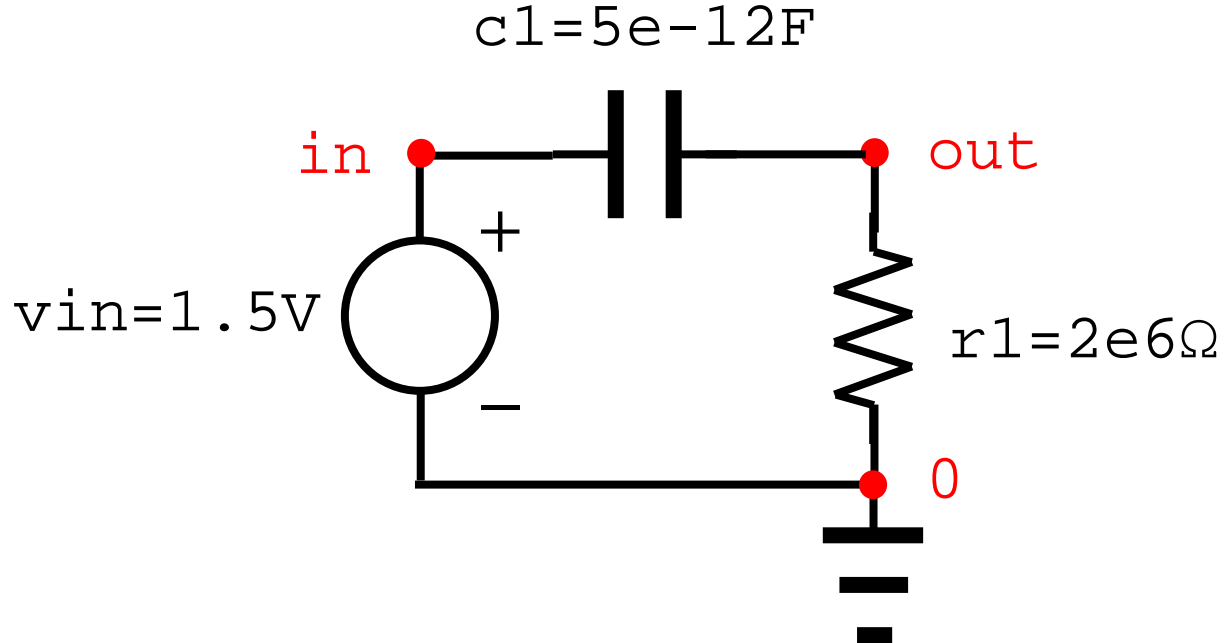

Circuit analysis (1)

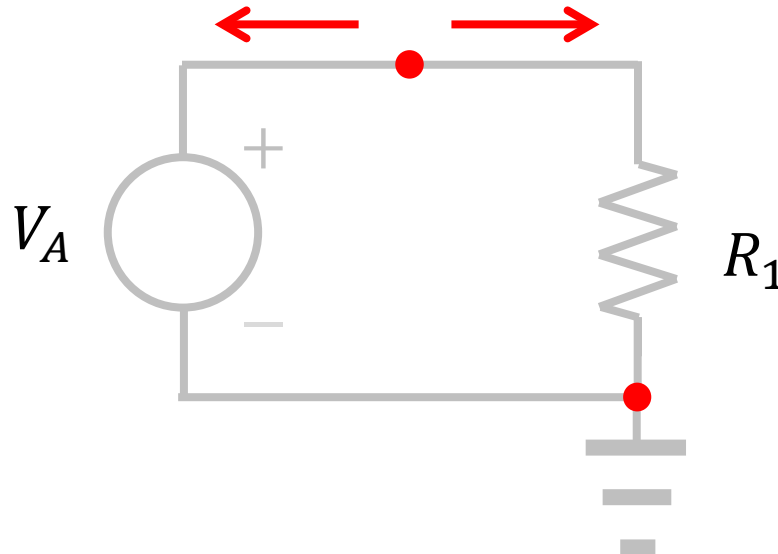- Kirchhoff's current law (KCL)!
 - At any node in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.



Circuit analysis (2)

- Our simple problem
 - Three equations:

Voltage source


$$V(out) - 0.0 = 1.0$$

$$I_{r1} = \frac{V(out)}{1000}$$

Resistor

$$I_{va} + I_{r1} = 0$$

KCL

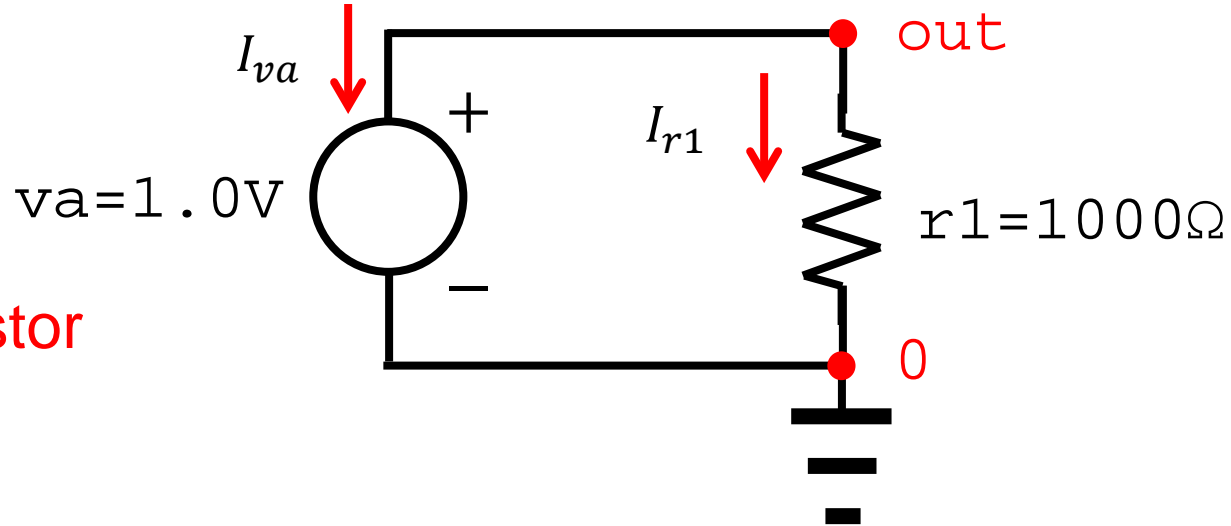

Implementation?

- Solution vector, $[I_{va} \quad I_{r1} \quad V(out)]^T$

- Then, the system is written as


$$\begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & -0.001 \\ 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} I_{va} \\ I_{r1} \\ V(out) \end{bmatrix} = \begin{bmatrix} 1.0 \\ 0 \\ 0 \end{bmatrix}$$

- The solution is

$$\begin{bmatrix} I_{va} \\ I_{r1} \\ V(out) \end{bmatrix} = \begin{bmatrix} -0.001 \\ +0.001 \\ 1.0 \end{bmatrix}$$

RC circuit

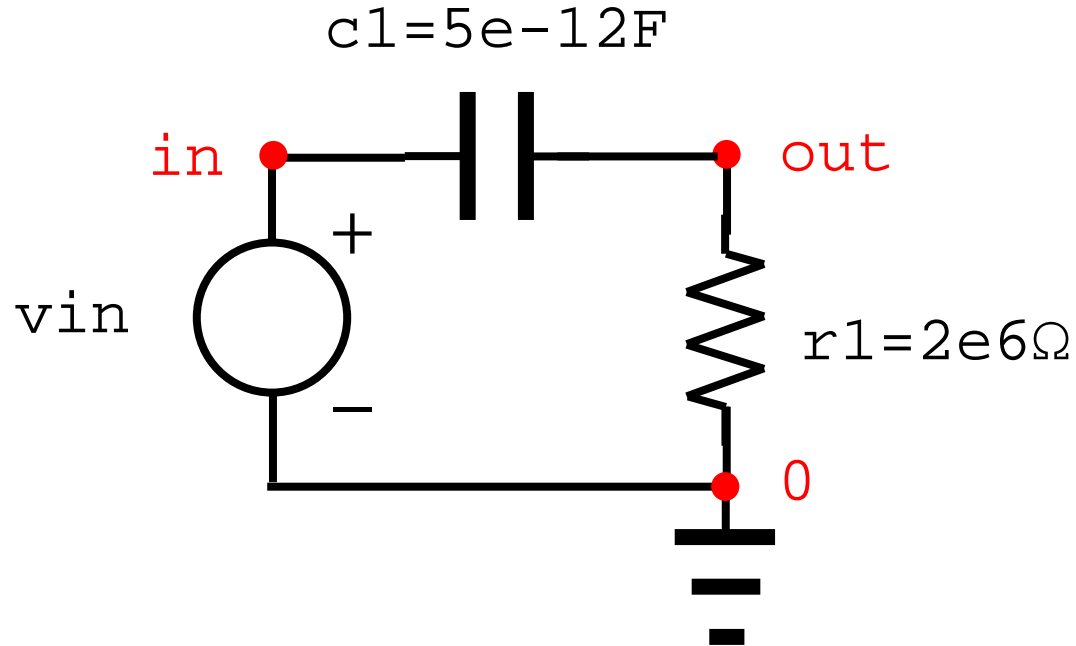- Solve a simple transient problem by a numerical means.



Frequency domain

- At a frequency, f , the impedance of the RC part is $Z(\omega) = R + \frac{1}{j\omega C}$ ($\omega = 2\pi f$)

– Therefore,

$$I(\omega) = \frac{V(\omega)}{Z(\omega)} = \frac{V(\omega)}{R + \frac{1}{j\omega C}} = \frac{j\omega C + \omega^2 R C^2}{1 + (\omega RC)^2} V(\omega)$$

– For example, when $V(t) = V_0 \cos \omega t$,

$$I(t) = \frac{\omega^2 R C^2}{1 + (\omega RC)^2} V_0 \cos \omega t - \frac{\omega C}{1 + (\omega RC)^2} V_0 \sin \omega t$$

Circuit analysis

- Five equations

- Two KCL's

$$I_{vin} + I_{c1} = 0$$


$$-I_{c1} + I_{r1} = 0$$

- Three equations

$$V(in) - 0.0 = \cos \omega t$$

$$I_{c1} = 5 \times 10^{-12} \frac{d}{dt} [V(in) - V(out)]$$
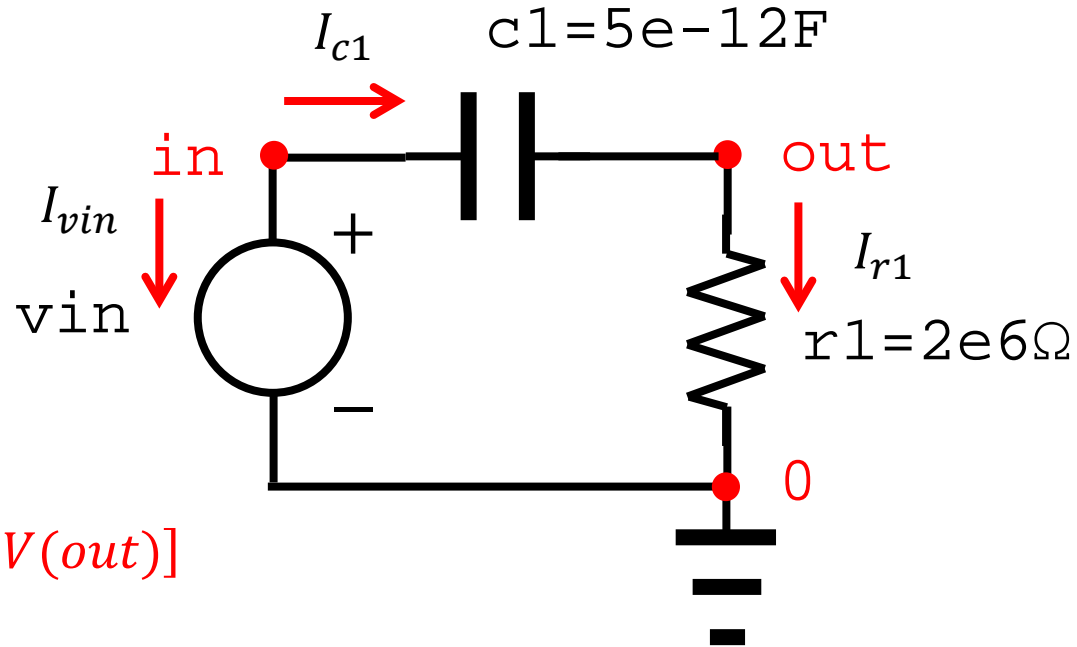
$$I_{r1} = \frac{V(out) - 0.0}{2 \times 10^6}$$



Implementation?

- Solution vector, $[I_{vin} \ I_{c1} \ I_{r1} \ V(in) \ V(out)]^T$

– Then, the system is written as

$$\begin{bmatrix} 0 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & -R^{-1} \\ 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -C & C \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \frac{d}{dt} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix} = \begin{bmatrix} \cos \omega t \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Backward Euler

- An implicit method
 - Uniform time discretization, $t_i = i\Delta t$
 - The time derivative at t_i is assumed to be

$$\frac{d}{dt} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix}_{t=t_i} = \frac{1}{\Delta t} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix}_{t=t_i} - \frac{1}{\Delta t} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix}_{t=t_{i-1}}$$

Discretized form

- By using the backward Euler method,
 - Then, the system is written as

$$\begin{bmatrix} 0 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & -C/\Delta t & C/\Delta t \\ 0 & 0 & 1 & 0 & -R^{-1} \\ 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix}_{t=t_i} + \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & C/\Delta t & -C/\Delta t \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{vin} \\ I_{c1} \\ I_{r1} \\ V(in) \\ V(out) \end{bmatrix}_{t=t_{i-1}} = \begin{bmatrix} \cos \omega t \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

MATLAB (1)

- RC filter
 - First, define some constants.

```
R = 2e6; % Ohm
```

```
C = 5e-12; % F
```

```
freq = 1e0; % Hz
```

```
deltat = 1/freq/100; % 0.01 of a period
```

- The system matrix

```
A = zeros(5,5);
```

```
A(1,:) = [0 0 0 1 0];
```

```
A(2,:) = [0 1 0 -C/deltat C/deltat];
```

```
A(3,:) = [0 0 1 0 -1/R];
```

```
A(4,:) = [1 1 0 0 0];
```

```
A(5,:) = [0 -1 1 0 0];
```

MATLAB (2)

- RC filter (Continued)

```
b = zeros(5,1);  
solution = [0 0 0 1 0]';  
N = 1000;  
for ii=1:N  
    t = ii*deltat;  
    solution_old = solution;  
    b(1,1) = cos(2*pi*freq*t);  
    b(2,1) = -C/deltat*(solution_old(4,1)-solution_old(5,1));  
    solution = A \ b;  
end
```